

Lab Experiment #2

Realization of Digital circuits using behavioral and Switch level modelling

2.1 Objective: To realize the design of digital circuits in Verilog using behavioral and switch level modelling then simulating and synthesizing using EDA tools.

2.2 Software tools Requirement

Equipments:

Computer with Xilinx and Modelsim Software Specifications:

HP Computer P4 Processor – 2.8 GHz, 2GB RAM, 160 GB Hard Disk

Softwares: Synthesis tool: Xilinx ISE.

Simulation tool: ModelSim Simulator

2.3 Prelab Questions

(write pre lab Q & A in an A4 sheet)

1. Write the difference between initial and always block.
2. List the Reduction and Logical Operators.
3. Give the use of Blocking and Nonblocking statements.
4. Differentiate case, casex and casez statements.


2.4.1 Problem 1: Write a Verilog code to implement Flip flops.

The following points should be taken care of:

1. Use If statement to design positive edge triggered D flip
2. Use case statement to design negative edge triggered T flip flop




Logic Diagram – Problem 1.1


Q	D	Q(T+1)
0	0	0
0	1	1
1	0	0
1	1	1

 

D flip flop

Logic Diagram – Problem 1.2

 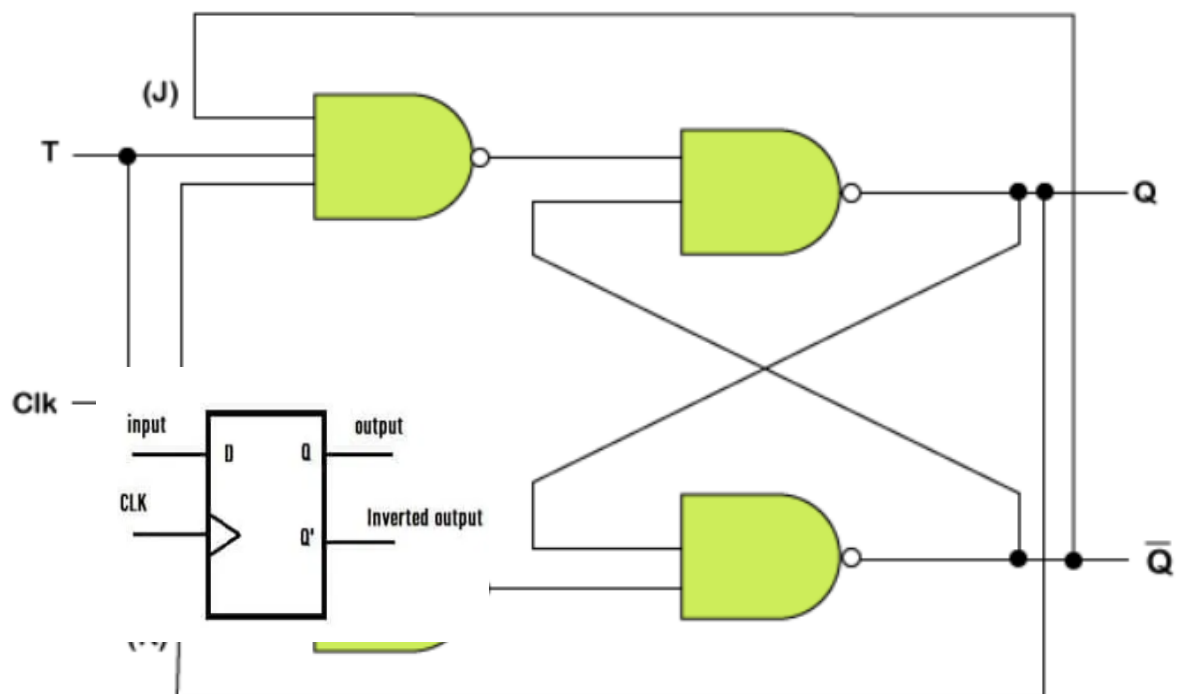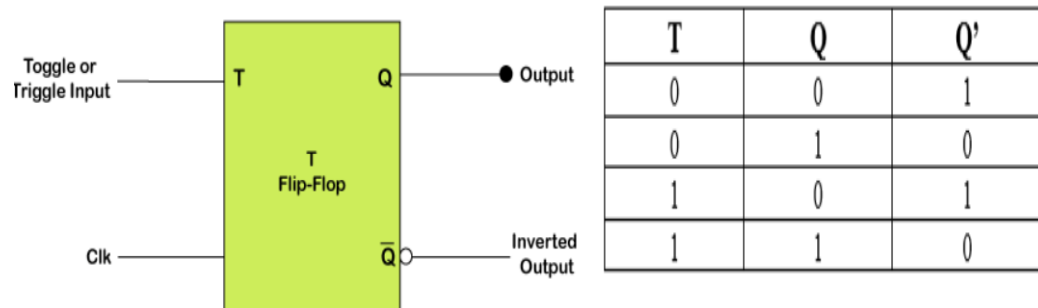

 

Verilog Code - Problem 1

1.(a) POSITIVE EDGE TRIGGERED D FLIPFLOP USING IF STATEMENT

```

module dff(q, qbar, d, clk, clear);
    output q;
    output qbar;
    input d;
    input clk;
    input clear;
    reg q, qbar;
    always@(posedge clk or posedge clear)
begin
    if(clear== 1)
    begin
        q <= 0;
        qbar <= 1;
    end
    else
    begin
        q <= d;
        qbar = !d;
    end
end
endmodule

```

// TEST BENCH

```

module dff_tb_v;

    // Inputs
    reg d;
    reg clk;
    reg clear;

    // Outputs
    wire q;

```

```

    wire qbar;

    // Instantiate the Unit Under Test (UUT)
    dff uut (
        .q(q),
        .qbar(qbar),
        .d(d),
        .clk(clk),
        .clear(clear)
    );

    initial begin
        // Initialize Inputs
        d = 0; clk = 0; clear = 1;

        // Wait 100 ns for global reset to finish
        #100 d = 0; clear = 0;
        #100 d = 1; clear = 0;
        #100 d = 1; clear = 1;

        // Add stimulus here

    end
    always #50 clk=~clk;
endmodule

1.2) NEGATIVE EDGE TRIGGERED T FLIPFLOP USING CASE STATEMENT

module tffcase(q, clk, clr, t);

    output q;

    input clk;

    input clr;

    input t;

    reg q;

initial
    q=0;

    always@(negedge clk)
        begin
            case({clr,t})
                2'b10: q=0;

                2'b00: q=q;

                2'b01: q=~q;

            endcase
        end
end

endmodule

// TEST BENCH

```

```

module tffcase_tb_v;

    // Inputs

    reg clk; reg clr; reg t;

    //

    Outputs

    wire q;

    // Instantiate the Unit Under Test
    (UUT) tffcase uut
    (.q(q),.clk(clk),.clr(clr),.t(t)); initial begin

        // Initialize Inputs
        clk = 0; clr = 1; t =
        0;

        // Wait 100 ns for global reset to
        finish #100; clr=0;

        #100; clr=0; t=1;

        // Add stimulus here

    end
always

    #50 clk=~clk;

endmodule

```

Waveforms – Problem 1

 


Fig 1.1 D Flipflop using IF statement

 


Fig 1.2 T Flipflop using CASE statement

2.4.2 Problem 2: Write a Verilog code to implement Counters.

The following points should be taken care of:

1. Use behavioral model to design Up-Down Counter. When mode = '1' do up counting and for mode = '0' do down counting.
2. Use behavioral model to design Mod-N counter.
3. Design SISO register using behavioral model.

Logic Diagram – Problem 2

Verilog Code - Problem 2

2.(1) UP DOWN COUNTER USING BEHAVIOURAL MODEL

```
module updowncntr(q, clr, clk, mod);
```

```
output reg [3:0] q;
```

```
input clr;
```

```
input clk;
```

```
input mod;
```

always@(posedge clk)

begin

```
case({clr,mod})
```

2'b11 : q=0;

2'b10 : q=0;

```
2'b01 : q=q+1;
```

```
2'b00 : q=q-1;
```

endcase

end

```

endmodule

// TEST BENCH

module updowncntr_tb_v;

    // Inputs
    reg clr; reg clk; reg mod;

    // Outputs
    wire [3:0] q;

    // Instantiate the Unit Under Test (UUT)
    updowncntr uut
    (.q(q),.clr(clr),.clk(clk),.mod(mod)); initial begin

        // Initialize Inputs
        clr = 1; clk = 0; mod = 1;

        // Wait 100 ns for global reset to
        finish #100; clr=0;

        #1000; mod=0;

        // Add stimulus here

    end

    always

        #50 clk=~clk;

Endmodule

```

2.(2) Mod N-COUNTER USING BEHAVIOURAL MODEL

```

module modN_ctr
# (parameter N= 10,
parameter WIDTH = 4)

( input  clk,
  input  rstn,
  output reg[WIDTH-1:0] out);

always @(posedge clk) begin
  if (rstn) begin
    out <= 0;
  end else begin
    if (out == N-1)
      out <= 0;
    else
      out <= out + 1;
    end
  end
end

```

```
endmodule
```

// TEST BENCH

```
module modncounter_tb_v;  
  
// Inputs  
reg clk;  
reg rstn;  
  
// Outputs  
wire [3:0] out;  
  
// Instantiate the Unit Under Test (UUT)  
modN_ctr uut (  
    .clk(clk),  
    .rstn(rstn),  
    .out(out)  
);  
  
initial begin  
    // Initialize Inputs  
    clk = 1; rstn = 1;  
  
    // Wait 100 ns for global reset to finish  
    #100 rstn=0;  
  
    // Add stimulus here  
  
end  
always #50 clk=~clk;  
endmodule
```


2.(3) SISO REGISTER USING BEHAVIOURAL MODEL

```
module siso_register(shift_out, shift_in, clk);  
input shift_in;  
input clk;  
output shift_out;  
reg shift_out;  
reg [2:0] data;  
always @(posedge clk)  
begin  
    data[0] <= shift_in ;  
    data[1] <= data[0];  
    data[2] <= data[1];  
    shift_out <= data[2];  
  
end  
  
endmodule
```

// TEST BENCH

```
module siso_tb_v;  
  
// Inputs  
reg shift_in;  
reg clk;  
  
// Outputs  
wire shift_out;  
  
// Instantiate the Unit Under Test (UUT)  
siso_register uut (  
    .shift_out(shift_out),
```



Waveforms – Problem 2

  

1. Design inverter logic using verilog switch level modeling and verify the simulation result using test bench.

2. Design two input CMOS NAND logic using verilog switch level modeling and verify the simulation result using testbench.
3. Design 2:1 Mux using CMOS switches and write verilog coding using switch level modeling and verify the simulation result.

Logic Diagram-Problem 1



2.4.3 Verilog Code - Problem 1

CMOS Inverter

```
module inverter(out,data);
output out;
input data;
supply1 vdd;
supply0 gnd;
pmos p1(out,vdd,data);
nmos n1(out,gnd,data);
endmodule
```

CMOS Inverter_TB

```
module inverter_tb_v;
reg data;
inverter uut (.out(out), .data(data));
initial begin
data = 0;
#100 data = 1;
end
endmodule
```

6.4 Waveforms – Problem 1

Fig 6.4.1 CMOS inverter

Logic Diagram-Problem 2

 


Fig Two input NAND

2.4.3 Verilog Code - Problem 2

CMOS NAND Logic

```
module nandcmos(out,a,b);
  wire t;
  output out;
  input a,b;
  supply1 vdd;
  supply0 gnd;
  pmos m1(out,vdd,a);
  pmos m2(out,vdd,b);
  nmos m3(out,t,a);
  nmos m4(t,gnd,b);
endmodule
```

CMOS NAND Logic_TB


```
module nandcmos_tb_v;
  reg a; reg b;
  wire out;
  nandcmos uut (
    .out(out), .a(a), .b(b)
  );
  initial begin
    a = 0; b = 0;
    #100 a = 0; b = 1;
    #100 a = 1; b = 0;
    #100 a = 1; b = 1;
  end
end
```

endmodule

2.4.3 Waveforms – Problem 2

Fig 2.4.3 Two input NAND

Logic Diagram-Problem 3

 

2:1 Mux USING cmos

2.4.3 Verilog Code - Problem 3

CMOS Mux 2X1

```
module cmos_mux(out,s,i1,i0);  
  output out;  
  input s,i0,i1;  
  wire sbar;  
  not n1(sbar,s);  
  cmos(oout,i0,sbar,s);  
  cmos(out,i1,s,bar);  
endmodule
```

CMOS Mux 2X1_TB

```

module cmos_mux_tb_v;
reg s;reg i1;reg i0;
wire out;
cmos_mux uut (.out(out), .s(s),
.i1(i1),.i0(i0));
initial begin
s = 0;i1 = 1;i0 = 0; #100;
s = 0;i1 = 0;i0 = 1; #100;
s = 1;i1 = 0;i0 = 1; #100;
s = 1;i1 = 1;i0 = 1;
end
endmodule

```

2.4.3 Waveforms – Problem 3

 


Fig 2.4.3 2X1 Multiplexer using CMOS

2.5 Post Lab :

Write a Verilog HDL Code to implement a SIPO and PIPO shift registers.

2.6 Result:

Thus, the design of Digital circuits using behavioral and Switch level modelling is simulated in Verilog and synthesized using EDA tools.